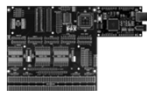




EEL 3744



Menu

- LED Array
 - > Raster Scan output device
 - > Example device
 - > Algorithm



EEL 3744

8x8 LED Array as a Graphic Display

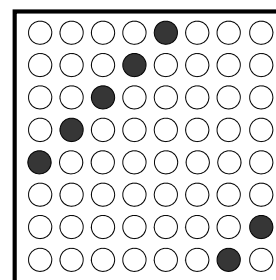
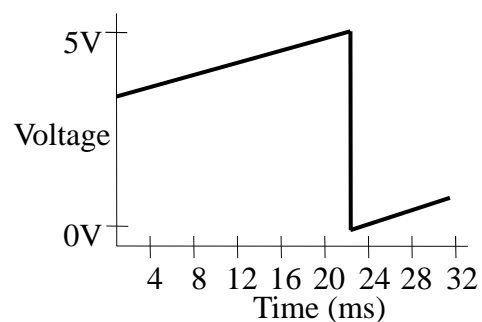


8x8 LED Array




EEL 3744

8x8 LED Array as a Graphic Display

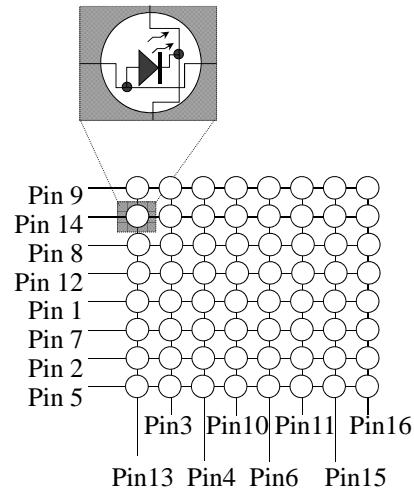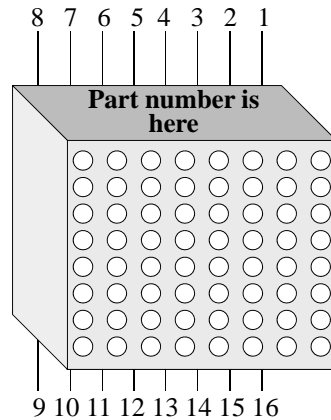


University of Florida, EEL 3744 – File 00
© Dr. Eric M. Schwartz

3

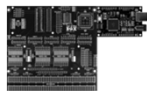

EEL 3744

8x8 LED Array as a Graphic Display

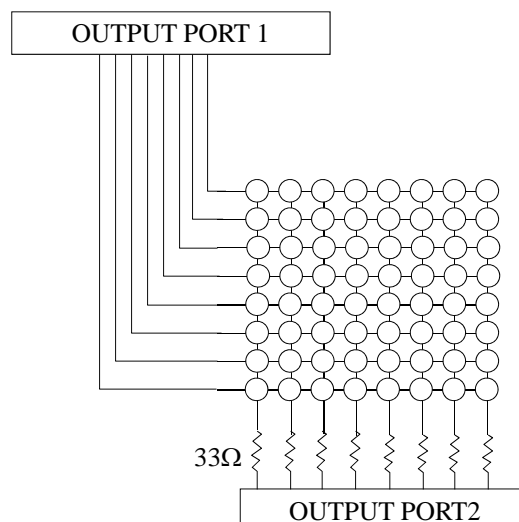

University of Florida, EEL 3744 – File 00
© Dr. Eric M. Schwartz


4




EEL 3744

Raster Scan LED Array

Example: Column Displays

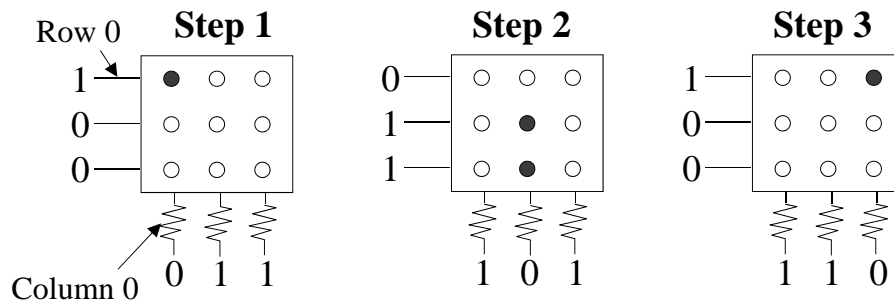


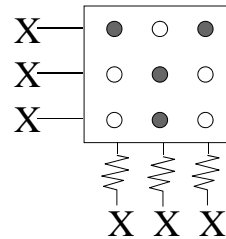- Appearance while looping from steps 1-3
- The LEDs are dimmer here than in steps 1-3



University of Florida, EEL 3744 – File 00
© Dr. Eric M. Schwartz

5

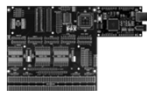

EEL 3744

The End!

University of Florida, EEL 3744 – File 00
© Dr. Eric M. Schwartz

6